


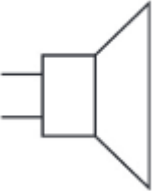


Electrical systems questions

1. Complete the table (5)

Component	Schematic Symbol	Function
Battery		It provides power to the circuit
Switch		
Lamp		
Motor		
		Converts electrical energy into sound

2. Draw a schematic drawing of the electrical circuit shown below. Label all the components (4)

